

POWER SUPPLY PROJECT CALCULATIONS

Prepared & Designed by Ali Hassan

Calculation for transformer:-

$$\text{As } \frac{N_s}{N_p} = \frac{V_s}{V_p}$$

As we know

$$V_p = 220\text{V}$$

$$V_s = 12\text{V}$$

$$\frac{N_s}{N_p} = \frac{12}{220}$$

$$\boxed{\frac{N_s}{N_p} = \frac{3}{55}}$$

Calculation before diode (Bridge Rectifier)

As we know $V_s = V_{rms}$

So $\boxed{V_{rms} = 12\text{V}}$

$$\text{As } V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

So $V_{max} = V_{rms} \times \sqrt{2}$
 $= 12 \times \sqrt{2}$

$$\boxed{V_{max} = 16.97\text{V}}$$

$$V_{dc} = \frac{2 V_{max}}{\pi}$$
$$= \frac{2 \times 16.97}{(3.14)}$$

$$\boxed{V_{dc} = 10.81\text{V}}$$

Calculation after bridge rectifier

Diode we use **1N5408**

Rating:-

Peak Reverse Voltage = 1000v

Maximum RMS Voltage = 700v

Forward Current = 3A

Voltage drop across each diode $\approx 0.7v$

$$\text{So } V_{\max} \text{ after diode} = V_{\max} - 2 \times 0.7$$
$$= 16.97 - 2 \times 0.7$$

$$= 16.97 - 1.4$$

$$\boxed{V_{\max} \text{ after diode} = 15.57v}$$

Ripple factor:-

$$\gamma = \frac{V_{r, \text{rms}}}{V_{dc}}$$

Finding V_{rms} & V_{dc} for $V_{\max} 15.57v$:-

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{15.57}{\sqrt{2}}$$

$$\boxed{V_{\text{rms}} = 11.01v}$$

$$V_{dc} = \frac{2 V_{\max}}{\pi}$$

$$= \frac{2 \times 15.57}{(3.14)}$$

$$\boxed{V_{dc} = 9.92v}$$

$$V_{r,rms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$= \sqrt{11.01^2 - 9.92^2}$$

$$V_{r,rms} = 4.776$$

$$\gamma = \frac{V_{r,rms}}{V_{dc}}$$

$$\gamma = \frac{4.776}{9.92}$$

$$\gamma = 0.4814$$

$$\gamma = 48.1\%$$

Diode Rating :- { Diode we can use }

$$PIV = V_{max}$$

$$= 16.97$$

$$PIV \text{ rating} \geq 1.5 \times 16.97$$

$$\geq 25.4V (\text{min})$$

$$PIV \text{ rating} \geq 2 \times 16.97$$

$$\geq 33.94 (\text{better})$$

$$I_{d,max} = \frac{V_{max}}{R_L} = \frac{16.97}{680}$$

$$I_{d,max} = 24.9mA$$

$$I_{d,max} \text{ rating} \geq 1.5 \times 24.9$$

$$\geq 34.35mA (\text{min})$$

$$I_{d,max} \text{ rating} \geq 2 \times 24.9$$

$$\geq 49.8mA (\text{better})$$

Rating we need:

$$PIV = 25.4 - 33.94V$$

$$I_{d,max} = 34.35 - 49.8mA$$

Rating we have:

$$PIV = 1000V$$

$$I_{d,max} = 3A$$

Filter (Capacitor)

Capacitor we need for 5% ripple factor

$$C = \frac{1}{4\sqrt{3} \times r \times R_L \times f}$$
$$= \frac{1}{4\sqrt{3} \times 0.05 \times 680 \times 50}$$

$$C = 85 \mu F$$

But as we have $4700 \mu F$ capacitor so its ripple factor will be:-

$$\gamma = \frac{1}{4\sqrt{3} \times C \times R_L \times f}$$
$$= \frac{1}{4\sqrt{3} \times 4700 \times 680 \times 50}$$

$$\gamma = 0.0009$$

$$\gamma = 0.09\%$$

•————•

Calculation for Zener Diode:

Zener Diode we use is **BZV55-C12**
Rating from Data Sheet:-

$$\text{Zener Voltage} = V_Z = 12V$$

$$\text{Zener Voltage tolerance} = 5\%$$

$$\text{Power dissipation} = P_{\text{total}} = 500mW$$

$$V_{Z\text{min}} - V_{Z\text{max}} = 11.40 - 12.70$$

$$\text{Test current} = I_{ZT} = 5mA$$

$$\text{At } 5mA \text{ Zener Max Resistance} = Z_Z = 25\Omega$$

$$\text{Max Zener Current} = I_{ZM} = 42mA$$

$$\text{Forward voltage} = V_{f(\text{max})} = 0.9V$$

$$\text{Forward current} = I_{f(\text{max})} = 250mA$$

$V_{in(\text{min})} \Delta V_{in(\text{max})}$:-

$$\text{At } I_{ZK} = 5mA$$

$$V_{out} = V_Z - \Delta V_Z$$

$$= V_Z - (I_Z - I_{ZK}) Z_Z$$

$$= 12V - (5mA - 5mA) 25\Omega$$

$$V_{out} = 12V$$

$$V_{in(\text{min})} = I_{ZK} R + V_{out}$$

$$= (5mA)(270\Omega) + 12V$$

$$\boxed{V_{in(\text{min})} = 13.35V}$$

$$\text{At } I_{zm} = 42\text{mA}$$

$$\begin{aligned} V_{out} &= V_z + \Delta V_z \\ &= V_z + (I_{zm} - I_z) Z_z \\ &= 12\text{V} + (42\text{mA} - 5\text{mA}) 25\Omega \\ V_{out} &= 12.92\text{V} \end{aligned}$$

$$\begin{aligned} V_{in(max)} &= I_{zm} R + V_{out} \\ &= (42\text{mA})(270\Omega) + 12.92\text{V} \end{aligned}$$

$$V_{in(max)} = 24.26\text{V}$$

$R_L(\text{min})$:-

$$R_L(\text{min}) = \frac{V_{out}}{I_L(\text{max})}$$

$$I_L(\text{max}) = I_z(\text{max}) - I_z(\text{min})$$

$$I_z(\text{max}) = \frac{V_{in(\text{min})} - V_z}{R_z} = \frac{13.35 - 12}{270}$$

$$I_z(\text{max}) = \frac{V_{in(\text{max})} - V_z}{R_z} = \frac{24.26 - 12}{270}$$

$$I_z(\text{max}) = 42\text{mA}$$

$$I_L = 42\text{mA} - 5\text{mA} \Rightarrow I_L(\text{max}) = 37\text{mA}$$


$$R_L(\text{min}) = \frac{12}{37\text{mA}}$$

$$R_L(\text{min}) = 324\Omega$$

Power dissipation:

$$\begin{aligned} P_{z(\text{max})} &= V_z \times I_z \\ &= 12 \times 0.042 \end{aligned}$$

$$P_{z(\text{max})} = 0.5\text{W}$$

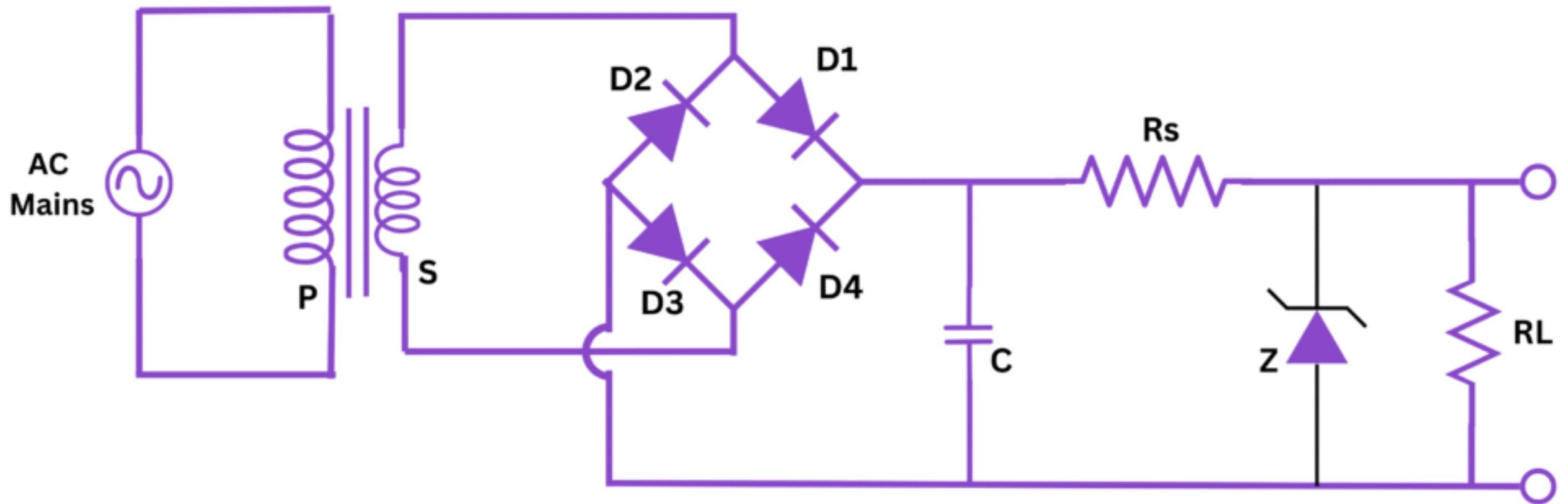

Prepared & Designed by Ali Hassan Ashraf